

## Overview

When high-speed clock and data systems have reached the bandwidth limits of single-ended CMOS/TTL logic, designers are forced to seek other logic alternatives. Today's high-speed emitter coupled logic (ECL), with true differential I/O and superior skew, jitter, and rise/fall times compared to LVTTTL logic, provide a compelling alternative. Positive ECL (ECL) is the most common ECL implementation method in today's low-voltage systems. PECL logic levels are referenced to the most positive rail (VCC), thus the translation from ECL-to-PECL is simple. PECL applies to 5V systems, while low-voltage PECL (LVPECL) applies to +2.5V and +3.3V systems. Micrel has an extensive logic and clock synthesis/generation family specified for PECL and LVPECL operation.

## Termination

As a result of ECL/PECLs differential, high input impedance, very low output impedance (Open Emitter), and small signal swing (and resulting low EMI), ECL/PECL is ideal for driving 50Ω and 100Ω controlled impedance transmission lines. A signal trace is considered a transmission line, thus requiring termination, when the signal's rise/fall time is faster than a trace's round-trip propagation delay. In some applications, if the distance between two devices is short enough, then termination may not be necessary. Another way to express this is:

If,  $t_{RISE(signal)} < 2 \times t_{PD(trace)}$ , then the trace is a transmission line and proper termination is required.

And, as with all high-speed transmission lines, to realize all the performance benefits of ECL/PECL, care must be observed when terminating. There are several PECL termination methods. Figures 1 through Figure 6 illustrate the different termination schemes. For optimal performance in high-frequency applications, Micrel recommends parallel termination (shown in Figure 3 and Figure 4). For fanning out to multiple locations, tapping off an existing output (driver) is not recommended because of the signal degradation caused by mismatches in the transmission lines. A better alternative is to use a Micrel fanout buffer such as an SY100EP11U or SY100EP111U. Micrel offers an extensive selection of high-frequency fanout buffers and translators, which can be found at the Micrel web site: [www.micrel.com](http://www.micrel.com).


## Unused I/O and Single-Ended Termination

Many applications will not use all of a device's outputs, such as a fanout buffer or translator. It is a common practice to terminate unused output pairs with a typical 2kΩ–4kΩ resistor to ground (PECL applications). In most cases, an unusual PECL/ECL output pair on a Micrel buffer, translator, or clock generator may be left floating (exceptions are noted in the datasheet).

For single-ended applications that only use one PECL output ( $Q_{OUT}$ ), the other output ( $I/Q_{OUT}$ ) must be terminated properly, as shown in Figure 6.


The circuit should have the same load on both outputs, even with single-ended applications. For single-ended input applications, the unused input must be set to the proper threshold level. The correct level for DC-coupled applications is  $V_{CC}-2V$ . The correct value for AC-coupled applications is  $V_{CC}-1.3V$  ( $V_{BB}$  equivalent). Many of Micrel's devices include a  $V_{BB}$  reference voltage pin; proper set-up is shown in Figure 6. If a  $V_{BB}$  reference is not available, a simple resistor network, as shown in Figure 6, should be implemented on the unused input.  $V_{BB}$  is intended for two applications-unused inputs (shown in Figure 6) and AC-coupled inputs. For AC-coupled inputs, the  $V_{BB}$  reference level ( $V_{CC}-1.3V$ ) is intended to be the termination point via 50Ω resistors on each input.

## Summary of Termination Techniques

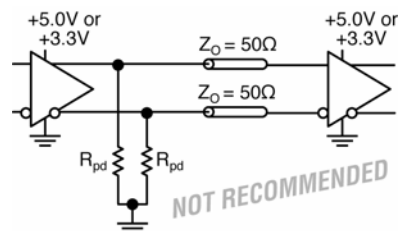


**Figure 1. No Termination**

- Typically not recommended due to overshoot/undershoot and reflections
- Only works for very short trace lengths,  $\ll 1''$  and low frequencies  $< 100\text{MHz}$
- Pull-down resistor ( $R_{pd}$ ) is required to set current drive for open-emitter outputs
- Pull-down resistor ( $R_{pd}$ ) is typically 180Ω to 250Ω

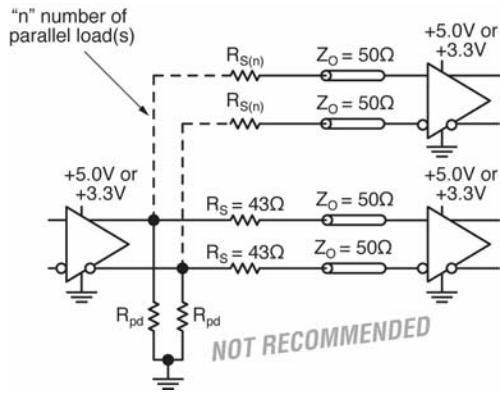

**Figure 2. Low-Frequency, Series Termination**


- Only for low-frequency applications <100MHz
- For long, uncontrolled impedance traces,  $R_S$  acts as series damping resistor
- $R_S \cong Z_O - \text{driver output impedance} = 50\Omega - 7\Omega \cong 43\Omega$
- $P_{pd} (\text{max}) = (10 \times Z_O - R_S)/n$ , where  $n$  is number of parallel loads
- Parallel loading is not recommended for high-frequency (>100MHz) applications. Instead, use a Micrel fanout buffer such as the SY100EP11U or SY100EP111U

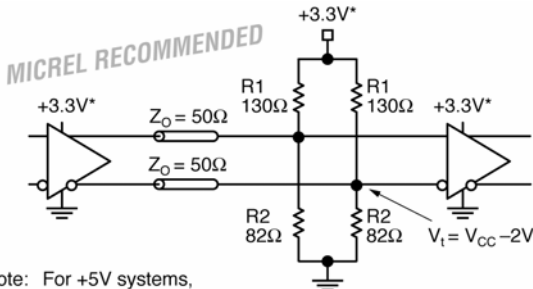

\*Note: For +5V systems, R1 = 82Ω, R2 = 130Ω


**Figure 3. Parallel Termination (Thevenin Equivalent)**

- Micrel recommended termination
- Most common PECL/LVPECL termination method
- Resistor divider tracks power-supply fluctuations
- For +3.3V systems,  $R1 = 2.5 \times Z_O$ ,  $R2 = 1.67 \times Z_O$
- For +2.5V systems,  $R1 = 1.67 \times Z_O$ ,  $R2 = 2.5 \times Z_O$
- Place termination as close to the destination pins as possible
- For parallel loading applications, use Micrel fanout buffer such as SY100EP11U or SY100EP111U

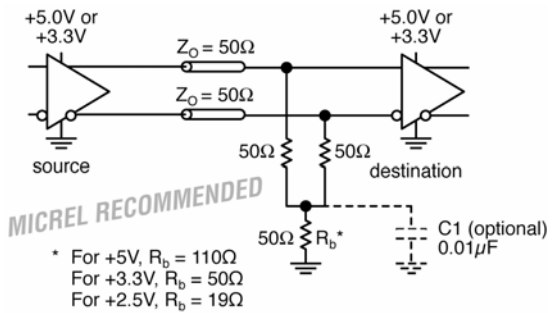

**Figure 4. Parallel Termination (3-Resistor)**

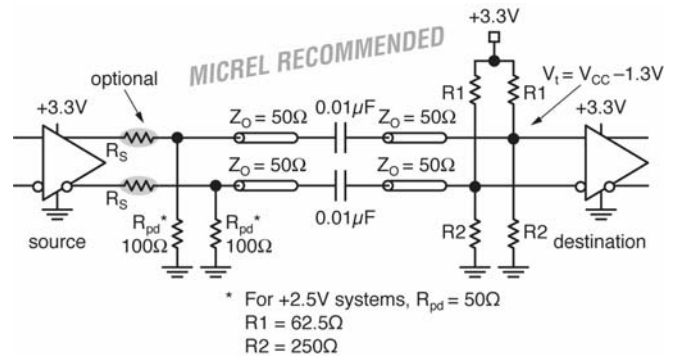
- Power saving alternative to 4-resistor, Thevenin termination
- Place termination resistors as close to destination inputs as possible
- $R_b$  resistor sets the DC bias voltage, equal to  $V_t$
- 3-resistor networks exist: small package, 1% accuracy, low cost: [www.thinfilm.com](http://www.thinfilm.com).



\* For +2.5V systems,  $R_{pd} = 50\Omega$   
 $R1 = 62.5\Omega$   
 $R2 = 250\Omega$

**Figure 5. Termination AC-Coupled Transmission Lines**

- AC-coupling is only recommended for clock applications (50% duty cycle)
- For best  $t_r/t_f$  performance, AC-coupling capacitors should be low ESR, low inductance at targeted clock frequency
- If ringing occurs (overshoot/undershoot), adding a series resistor ( $R_S$ ) will dampen the ringing. Typical value is approximately 10Ω. Place resistors as close to source pins as possible.
- Since the AC capacitor blocks the “pull-down” effect of the emitter follower,  $V_t \cong V_{CC} - 1.3V$
- Typical termination values for +3.3V systems are:
  - $R1 = 1k\Omega$
  - $R2 = 1.6k\Omega$
- If a  $V_{BB}$  reference is included, terminate each AC-coupling input with 50Ω to  $V_{BB}$ . Bypass the  $V_{BB}$  pin with a 0.01μF capacitor to  $V_{CC}$ , as PECL is referenced to  $V_{CC}$

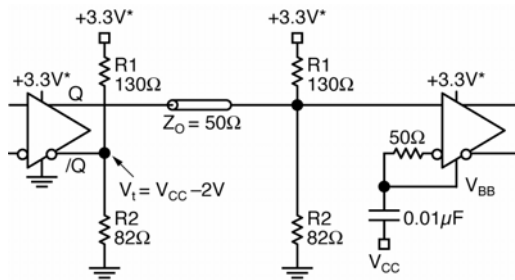

**Figure 6. Terminating Unused I/O**

- Unused output (/Q) must be terminated to balance output
- Micrel's differential I/O logic devices include a  $V_{BB}$  pin  
 $V_{BB} \cong V_{CC} - 1.3V$
- Connect unused input through  $50\Omega$  to  $V_{BB}$ . Bypass with a  $0.01\mu F$  capacitor to  $V_{CC}$ , not GND, as PECL is referenced to  $V_{CC}$ .

Datasheets and support documentation can be found on Micrel's web site at: [www.micrel.com](http://www.micrel.com).

**MICREL, INC. 2180 FORTUNE DRIVE SAN JOSE, CA 95131 USA**  
 TEL +1 (408) 944-0800 FAX +1 (408) 474-1000 WEB <http://www.micrel.com>

The information furnished by Micrel in this data sheet is believed to be accurate and reliable. However, no responsibility is assumed by Micrel for its use. Micrel reserves the right to change circuitry and specifications at any time without notification to the customer.

Micrel Products are not designed or authorized for use as components in life support appliances, devices or systems where malfunction of a product can reasonably be expected to result in personal injury. Life support devices or systems are devices or systems that (a) are intended for surgical implant into the body or (b) support or sustain life, and whose failure to perform can be reasonably expected to result in a significant injury to the user. A Purchaser's use or sale of Micrel Products for use in life support appliances, devices or systems is a Purchaser's own risk and Purchaser agrees to fully indemnify Micrel for any damages resulting from such use or sale.

© 2006 Micrel, Incorporated.